

Modification to run CPU09CMI on 4.5MHz bus.

Now we need the Q clock on the 09FLP

Replace xtal into 18MHz.

Replace C1 and C2 by 15pF.

Place 10M smd between crystal pins.

Replace GAL CMI_1 by CMI-4_1


Only use the HD63C09.

Skip next if already on 16Mhz modification!

On top side:

Cut trace between U4-14 and J1 C-21 (B_VMA-)

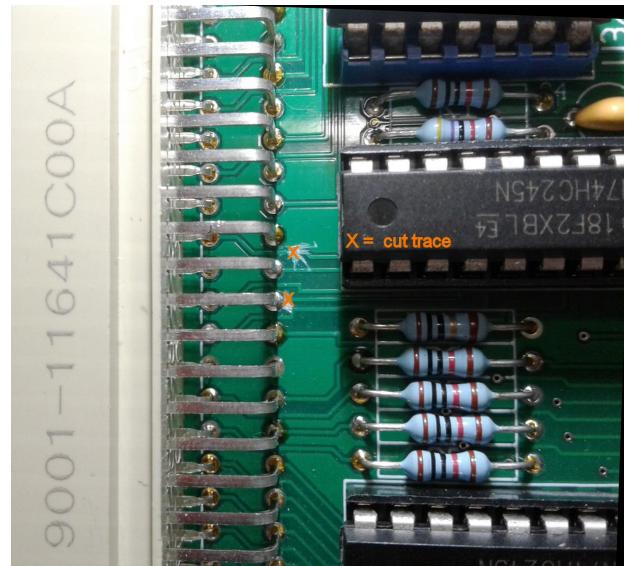For REV:0.9 print only cut trace from J1 A23 to R15




On solder side:

Cut trace between U13-19 and via (OVMA-)

Place 22K resistor between U13-19 and Gnd

Place wire from U6-35 to U13-19 (blue) and U4-6 (Q) (yellow)

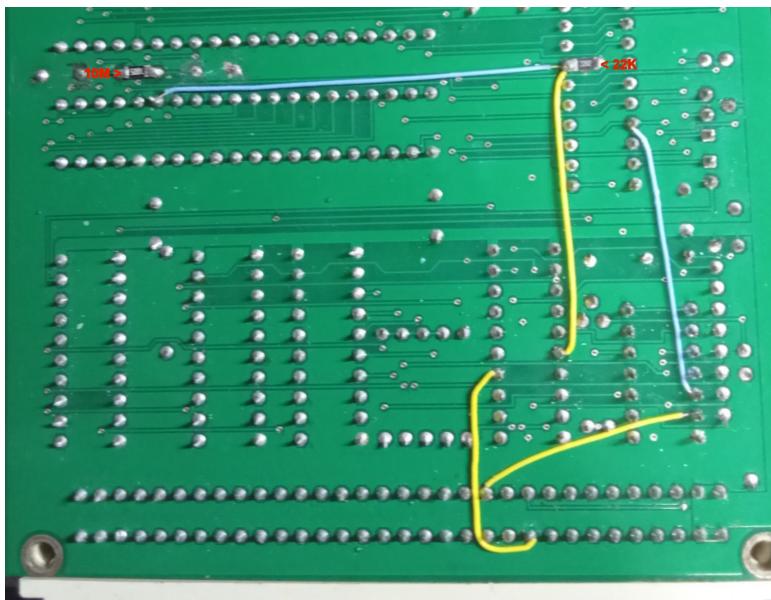Place wire from U4-14 to J1 A-23 (B_Q) (yellow)



Place wire from U3-7 to J1 C-21 (B_VMA-) , Or:

**To keep CPU09CMI 68x02 compatible
or need VMA- signal with 68x02 on the bus
for CPU09GPP or CPU09RAM card.**


On top side:

Cut trace between U3-4 and U3-5

On solder side:

Place wire from U3-5 to U13-9 (VMA) (blue)

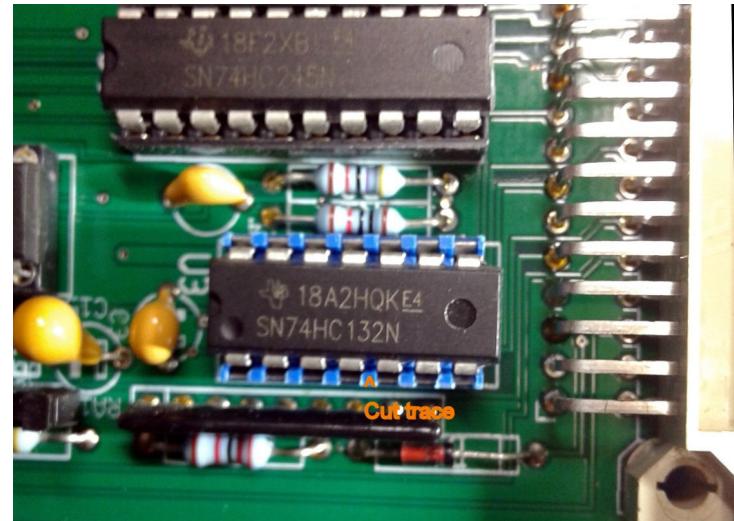Place wire from U3-6 to J1 C-21 (B_VMA-) (yellow)



Remarks:

Works with MC6850, MC68B50, HD6350, HD63B50.

CPU09RAM, CPU09IDE works fine. FLXMIN + 09FLP read FLP_MRDY.

Should work on REV:0.9 and REV:1.1 print

With xtal up to 12 MHz and correct GAL's the S6802, MC68B02 still works on this board.